

Stabilizing switching control of power converters: the lossy line and nonlinear case

Marius Zainea[†], Arjan van der Schaft[‡], Jean Buisson[†]

[†]Supelec-IETR Rennes, Hybrid Systems Control Group, France

[‡]Dept. of Mathematics, University of Groningen, The Netherlands

1. Port-Hamiltonian representation of power-converters
2. Controlled equilibria and Lyapunov functions
3. The transmission line as a port-Hamiltonian system
4. Power converter + transmission line + load

This work was partially supported by HYCON.

Port-Hamiltonian representation of power converters

Example: *Boost converter*

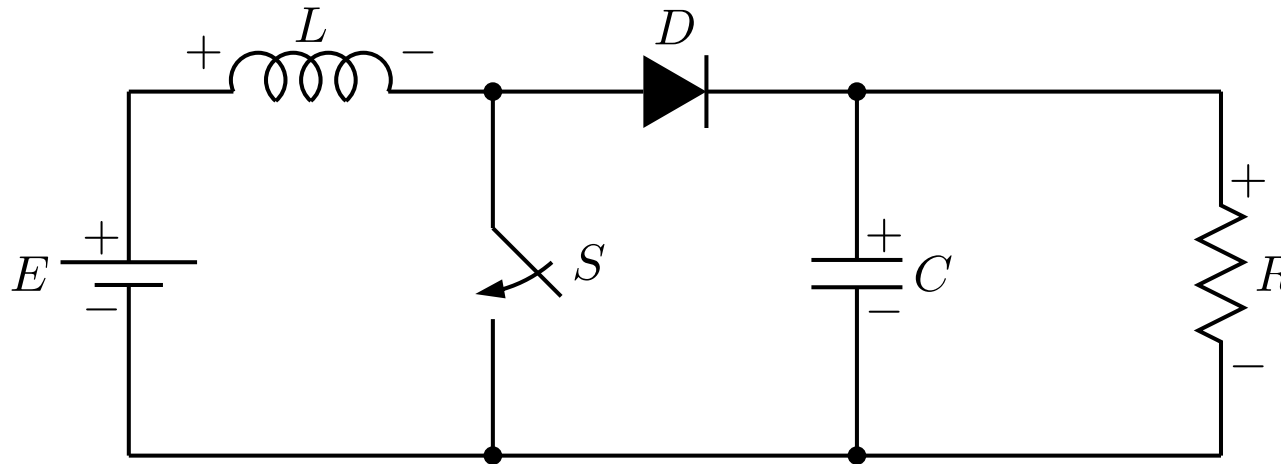


Figure 1: Boost circuit with clamping diode

The circuit consists of a capacitor C with electric charge q_C , an inductor L with magnetic flux linkage ϕ_L , and a resistive load R , together with an ideal diode and an ideal switch S , with switch positions $s = 1$ (switch closed) and $s = 0$ (switch open).

The voltage-current characteristics of the ideal diode and switch are depicted in Figure 2.

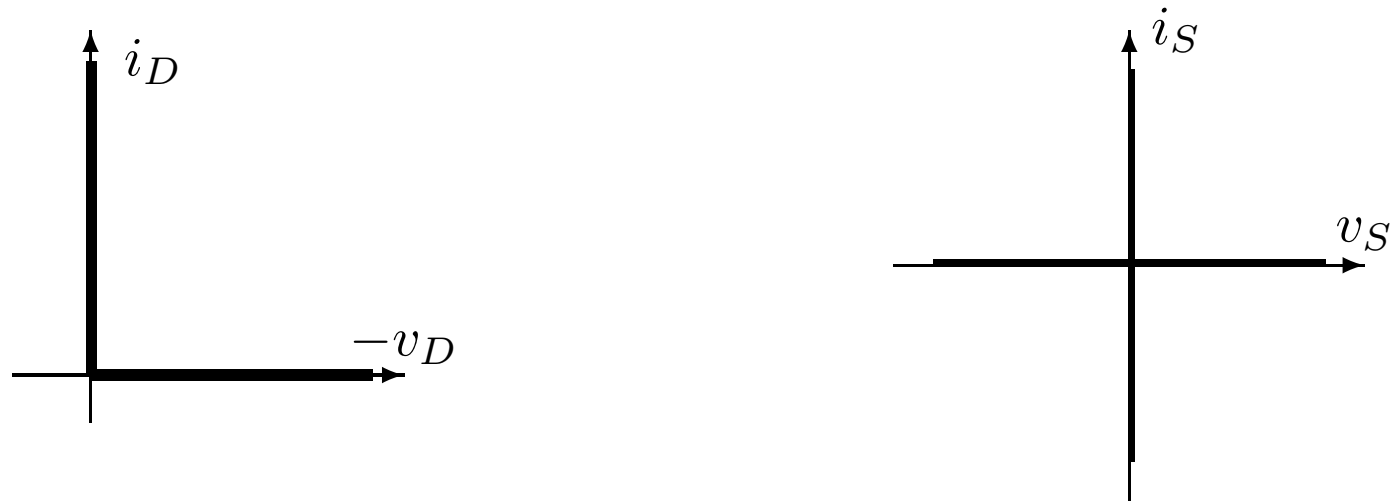


Figure 2: Voltage-current characteristic of an ideal diode and ideal switch

The ideal diode thus satisfies the complementarity conditions:

$$v_D i_D = 0, \quad v_D \leq 0, \quad i_D \geq 0.$$

This yields the port-Hamiltonian model (with

$$H(q_C, \phi_L) = \frac{1}{2C} q_C^2 + \frac{1}{2L} \phi_L^2):$$

$$\begin{bmatrix} \dot{q}_C \\ \dot{\phi}_L \end{bmatrix} = \begin{bmatrix} -\frac{1}{R} & 1-s \\ s-1 & 0 \end{bmatrix} \begin{bmatrix} \frac{\partial H}{\partial q_C} = \frac{q_C}{C} \\ \frac{\partial H}{\partial \phi_L} = \frac{\phi_L}{L} \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} E + \begin{bmatrix} s i_D \\ (s-1) v_D \end{bmatrix}$$

$$I = \frac{\phi_L}{L}$$

By disregarding the 'discontinuous modes' (*normal operation*), that is, assuming that when the switch is closed ($s = 1$) the diode is open ($i_D = 0$), while if the switch is open ($s = 0$) the diode is closed ($v_D = 0$),

we obtain the *switching port-Hamiltonian system*

$$\begin{bmatrix} \dot{q}_C \\ \dot{\phi}_L \end{bmatrix} = \begin{bmatrix} -\frac{1}{R} & 1-s \\ s-1 & 0 \end{bmatrix} \begin{bmatrix} \frac{\partial H}{\partial q_C} = \frac{q_C}{C} \\ \frac{\partial H}{\partial \phi_L} = \frac{\phi_L}{L} \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} E$$

$$I = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} \frac{\partial H}{\partial q_C} = \frac{q_C}{C} \\ \frac{\partial H}{\partial \phi_L} = \frac{\phi_L}{L} \end{bmatrix} = \frac{\phi_L}{L}$$

In general, a switching port-Hamiltonian system without algebraic equality and inequality constraints is defined as

$$\dot{x} = F(\rho)z + g(\rho)u, \quad z = \frac{\partial H}{\partial x}(x)$$

$$y = g^T(\rho)z$$

with

$$F(\rho) = J(\rho) - R(\rho), \quad J(\rho) = -J^T(\rho), \quad R(\rho) = R^T(\rho) \geq 0$$

Note that the system is passive for every switching sequence:

$$\frac{d}{dt}H = -\frac{\partial^T H}{\partial x}(x)R(\rho)\frac{\partial H}{\partial x}(x) + u^T y \leq u^T y$$

Basic property of power converters in normal operation

Consider the port-Hamiltonian representation

$$\begin{aligned}\dot{x} &= F(\rho)z + g(\rho)E + g_l u, & z &= \frac{\partial H_p}{\partial x}(x) \\ y &= g_l^T z\end{aligned}$$

with vector of Boolean variables $\rho \in \{0, 1\}^p$, $H_p(x)$ the total stored electromagnetic energy, and (u, y) the current-voltage pair over the resistive load.

Let x_0 be an equilibrium of the *averaged* model, that is

$$F(\rho_0)z_0 + g(\rho_0)E + g_l u_0 = 0, \quad z_0 = \frac{\partial H_p}{\partial x}(x_0)$$

for some $\rho_0 \in [0, 1]^p$ and u_0 . Then

$$\begin{aligned} \dot{x} &= F(\rho)(z - z_0) + F(\rho)z_0 + g(\rho)E + g_l u \\ &= F(\rho)(z - z_0) + [F(\rho) - F(\rho_0)]z_0 + [g(\rho) - g(\rho_0)]E + g_l(u - u_0) \\ &\quad + F(\rho_0)z_0 + g(\rho_0)E + g_l u_0 \\ &= F(\rho)(z - z_0) + [F(\rho) - F(\rho_0)]z_0 + [g(\rho) - g(\rho_0)]E + g_l(u - u_0) \end{aligned}$$

For many power converters in normal operation we know that

$$\begin{aligned} F(\rho) - F(\rho_0) &= \sum_{i=1}^p F_i(\rho_i - \rho_{0i}) \\ g(\rho) - g(\rho_0) &= \sum_{i=1}^p g_i(\rho_i - \rho_{0i}) \end{aligned}$$

and thus

$$\dot{x} = F(\rho)(z - z_0) + \sum_{i=1}^p [F_i z_0 + g_i E](\rho_i - \rho_{0i}) + g_l(u - u_0)$$

Take as Lyapunov/storage function

$$V(x) := H_p(x) - (x - x_0)^T \frac{\partial H_p}{\partial x}(x_0) - H_p(x_0)$$

Then

$$\begin{aligned} \frac{d}{dt} V(x) &= \left[\frac{\partial H_p}{\partial x}(x) - \frac{\partial H_p}{\partial x}(x_0) \right]^T \dot{x} = (z - z_0)^T \dot{x} = (z - z_0)^T F(\rho)(z - z_0) \\ &\quad + \sum_{i=1}^p (z - z_0)^T [F_i z_0 + g_i E](\rho_i - \rho_{0i}) + (z - z_0)^T g_l(u - u_0) \end{aligned}$$

with $(z - z_0)^T F(\rho)(z - z_0) = -(z - z_0)^T R(\rho)(z - z_0) \leq 0$.

Thus at any time we can choose the Boolean variables $\rho_i \in \{0, 1\}$ in such a manner that

$$\frac{d}{dt}V(x) \leq (z - z_0)^T g_l(u - u_0)$$

implying passivity of the switched system with respect to the input vector $u - u_0$ and output vector $y - y_0 = g_l^T(z - z_0)$.

As a consequence, if the converter is terminated on a resistive load R (and hence the equilibrium x_0 should be such that $y_0 = -Ru_0$) then the switched converter is generally asymptotically stable around x_0 . Thus the voltage over the resistive load can be stabilized around any set-point. (For the linear case, cf. Buisson, Cormerais, Richard.)

Remark 1 *Note that for linear capacitors and inductors we have*

$$H_p(x) = \frac{1}{2}x^T Qx, \quad V(x) = \frac{1}{2}(x - x_0)^T Q(x - x_0)$$

Power converter connected to the load via transmission line

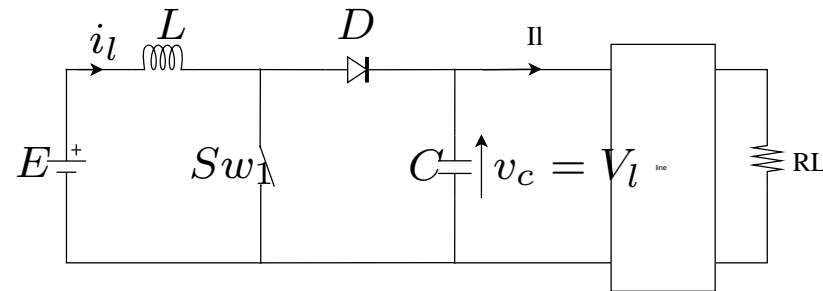


Figure 3: The Boost converter with a transmission line

Port-Hamiltonian representation of the transmission line

Let $s \in [0, 1]$ be the spatial variable. The energy variables are the charge density $Q = Q(t, s) ds$, and the flux density $\varphi = \varphi(t, s) ds$.

The total energy stored in the transmission line is

$$H_l(Q, \varphi) = \int_0^1 \frac{1}{2} \left(\frac{Q^2(t, s)}{C_l} + \frac{\varphi^2(t, s)}{L_l} \right) ds$$

where C_l and L_l are the distributed capacitance and inductance of the line. The voltage and current at any position $s \in [0, 1]$ are

$$V(t, s) = \frac{Q(t, s)}{C_l}$$
$$I(t, s) = \frac{\varphi(t, s)}{L_l}$$

The lossy transmission line is given by the telegrapher's equations

$$\begin{aligned}\frac{\partial Q}{\partial t} &= -\frac{\partial I}{\partial s} - G_l V(s, t) \\ \frac{\partial \varphi}{\partial t} &= -\frac{\partial V}{\partial s} - R_l I(s, t),\end{aligned}$$

where G_l and R_l are the distributed conductance and the distributed resistance of the line. Since the transmission line is terminated on a resistive load R_L

$$V(t, 1) = R_L I(t, 1)$$

while $V(t, 0)$ and $I(t, 0)$ is the voltage, respectively the current, at the beginning of the line, as to be connected to the voltage=current pair (y, u) of the power converter.

This is a port-Hamiltonian system satisfying

$$\frac{d}{dt} H_l \leq -R_L V^2(t, 1) + uy$$

Power converter + transmission line + load

The total system is a port-Hamiltonian system with Hamiltonian $H_p + H_l$.

An equilibrium $(V_0(s), I_0(s))$ for the line satisfies

$$\frac{\partial Q}{\partial t} = \frac{\partial \varphi}{\partial t} = 0,$$

and thus is a solution of

$$\begin{pmatrix} \frac{\partial V_0}{\partial s}(s) \\ \frac{\partial I_0}{\partial s}(s) \end{pmatrix} = \begin{pmatrix} 0 & -R_l \\ -G_l & 0 \end{pmatrix} \begin{pmatrix} V_0(s) \\ I_0(s) \end{pmatrix},$$

satisfying additionally the boundary condition

$$V_0(0) = y_0$$

$$V_0(0) = u_0$$

$$V_0(1) = R_L I_0(1)$$

An equilibrium of the system *power converter + transmission line + load* is thus given by (z_0, V_0, I_0) linked by certain u_0, y_0 (the equilibrium current and voltage at the left-end of the line).

Take as Lyapunov function of the total system

$$\begin{aligned} V(x, Q, \phi) &:= H(x) - (x - x_0)^T \frac{\partial H}{\partial x}(x_0) - H(x_0) \\ &+ H_l(Q - Q_0, \phi - \phi_0) \end{aligned}$$

It follows that

$$\begin{aligned} \frac{d}{dt}V &= (z - z_0)^T F(\rho)(z - z_0) + \sum_{i=1}^p (z - z_0)^T [F_i z_0 + g_i E](\rho_i - \rho_{0i}) \\ &- (V(t, 1) - V_0)^2 / R_L - \int_0^1 \left[(V - V_0)^2 G_l + (I - I_0)^2 R_l \right] ds \end{aligned}$$

and, as before, we can make the right-hand side negative by choice of the Boolean variables $\rho_i \in \{0, 1\}$ (depending only on the values of the state variables of the power converter).

Conclusions

1. Stabilizing switching control strategy for linear power converters has been extended to
 - Lossy transmission line between power converter and resistive load.
 - Nonlinear capacitors and inductors.
2. How to extend to nonlinear resistive elements ?
3. How to deal with discontinuous modes ?